

Switched Current Power Converter


a true breakthrough technology

Arnold Alderman
&
Edward Herbert

- Founder and President of Anagenesis, Inc., a technical marketing consulting firm located in Los Angeles and Phoenix
- 22 years engineering and management at Boeing, GE, and Emerson Electric and other US power conversion companies
- 16 years technical, product, and strategic marketing at Fairchild Semiconductor and International Rectifier
- Author of numerous conference papers and articles with publications in leading industry magazines, keynote speaker, plenary speaker
- Conducted marketing and technology seminars internationally.
- Board Chairperson of the Power Sources Manufacturing Association (PSMA)

- Inventor, 37 Issued Patents, several applications pending
- Held both design and engineering management positions at Dynamic Controls Corp., South Windsor, CT; IBM., Huntsville, Alabama; Sundstrand Aviation, Rockford, Illinois; Hamilton Standard, Windsor Locks, CT; Raytheon Submarine Signal Div., Portsmouth, RI; Sikorsky Aircraft, Stratford, CT.
- Power factor correction circuits in 2001
- Founder and President of FM TT Inc.
- Invented the Matrix transformer in late 80s

Wasted processor power

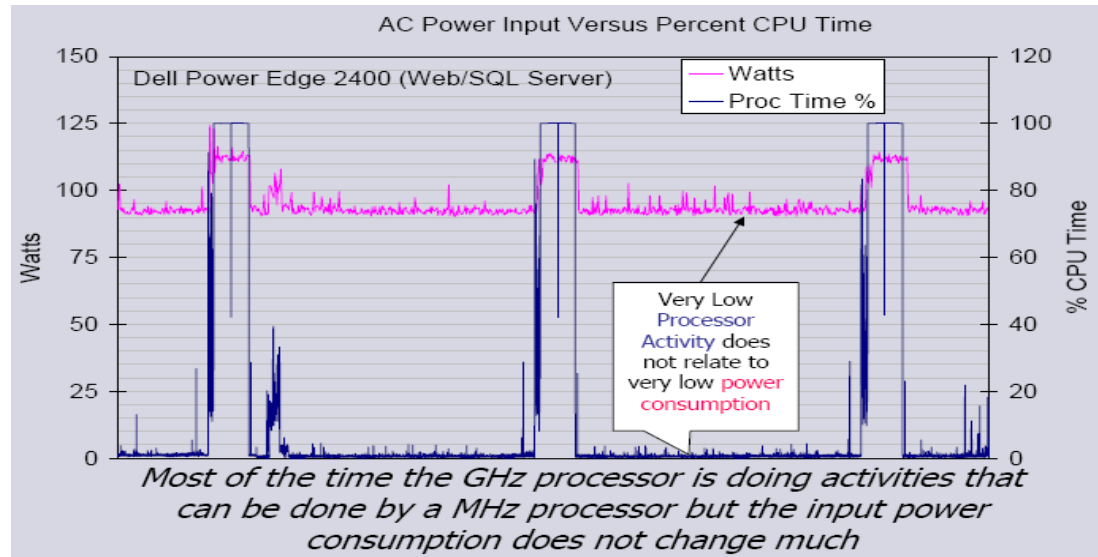


This processor is wasting power most of the time. *A power supply with very fast transition time allows the processor cores to be turned off most of the time, for very significant system power reduction.*

The greatest dividend for reducing system power comes from enabling the processor to operate at lower power most of the time.

*With the SCPC, the voltage can be:
ramped at up to $1500\text{ mv}/\mu\text{s}$,
turned off in $2\text{ }\mu\text{s}$,
and turned on to any VID voltage and
 100% current capability in $2\text{ }\mu\text{s}$.*


- The Switched Current Power Converter with Switched Charge Voltage Control is a true break-through technology providing:
 - *Fastest possible di/dt*
 - *Fastest possible dv/dt*
 - *Fastest possible transition times
(on, off, step voltage, or voltage ramp - up or down)*
 - *Expandable to multiple outputs*
 - *Very low standby power*

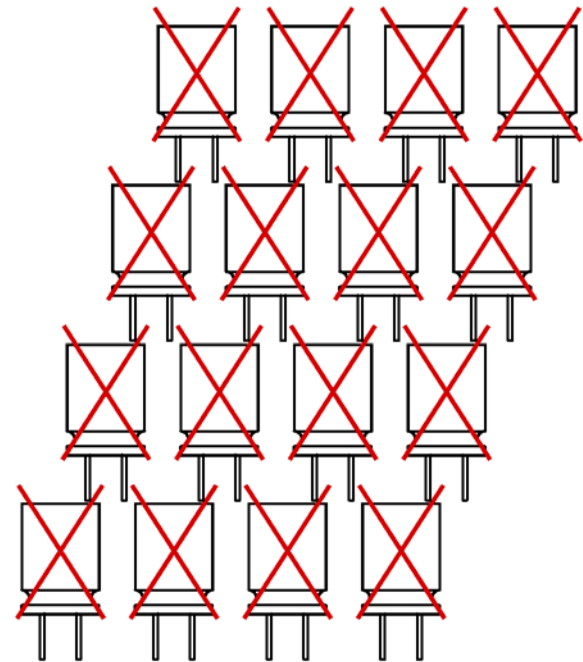- Saves power:
 - *Very fast dynamic response allows the processor to remain off or in lower power states for a greater percentage of the time*
- Saves board area:
 - *The bulk capacitors can be eliminated.*
- Saves cost:
 - *Trades-off capacitors for silicon*
 - *Less heat-sinking*




SCPC output impedance curve

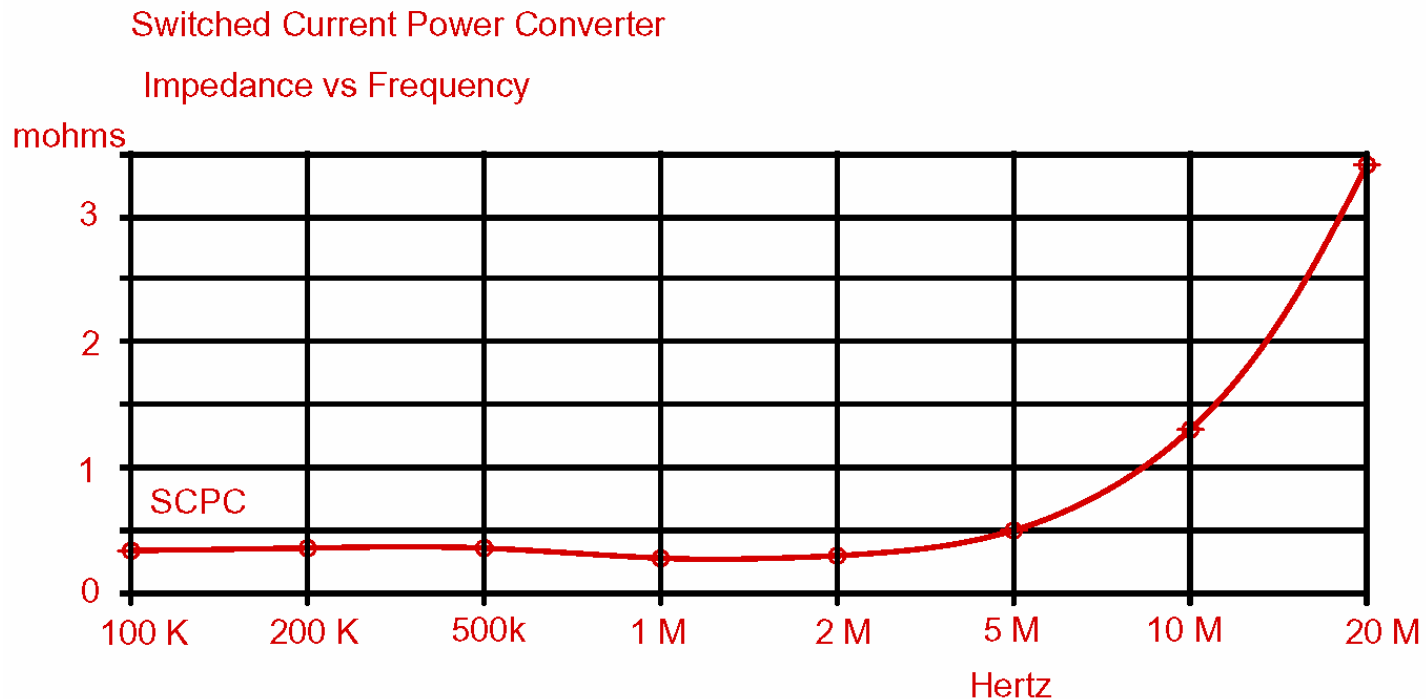- Dynamic and static impedance remains below 0.5 mΩ to 5 MHz.
- Model: 50 A_{pp} ac on 60 A dc (35 A to 85A);
- Load and parasitic impedances per VR 10.2.
- No bulk capacitors, only 500 μF MLCC.



SCPC step response

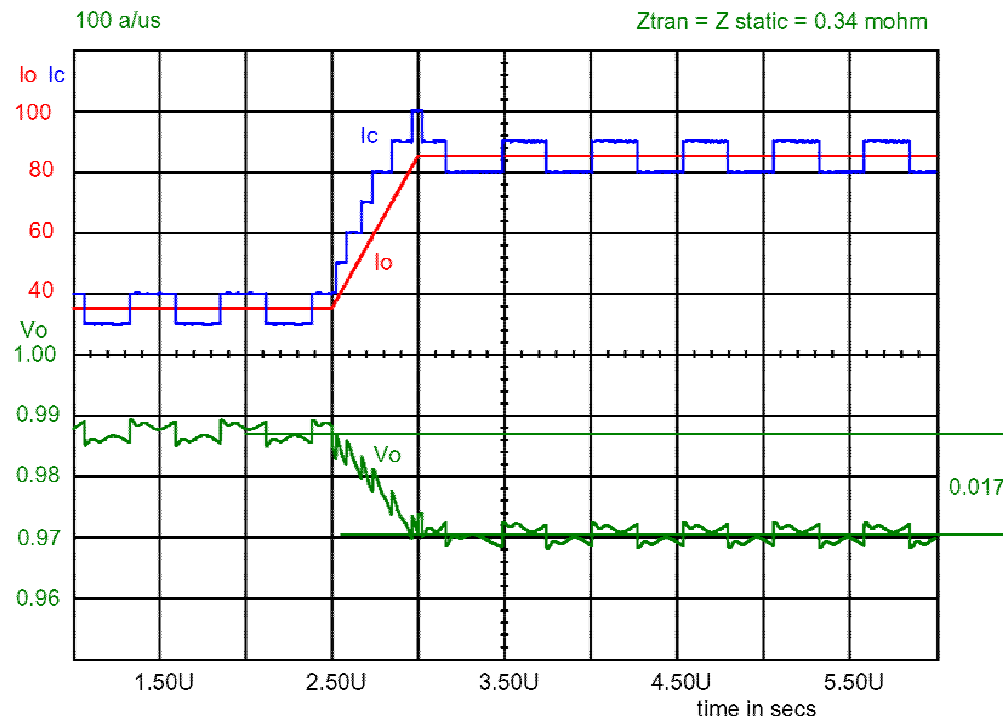- Current step is 35 A to 85 A, 100 A/ μ s
(Spice model load and parasitic impedances per VR 10.2.)
- *At 100 A/ μ s, the voltage V_o is regulated through the transient.*




Switched current power converter with binary switched charge.

(Spice model load and parasitic impedances per VR 10.2.)

Binary Switched Charge SCPC

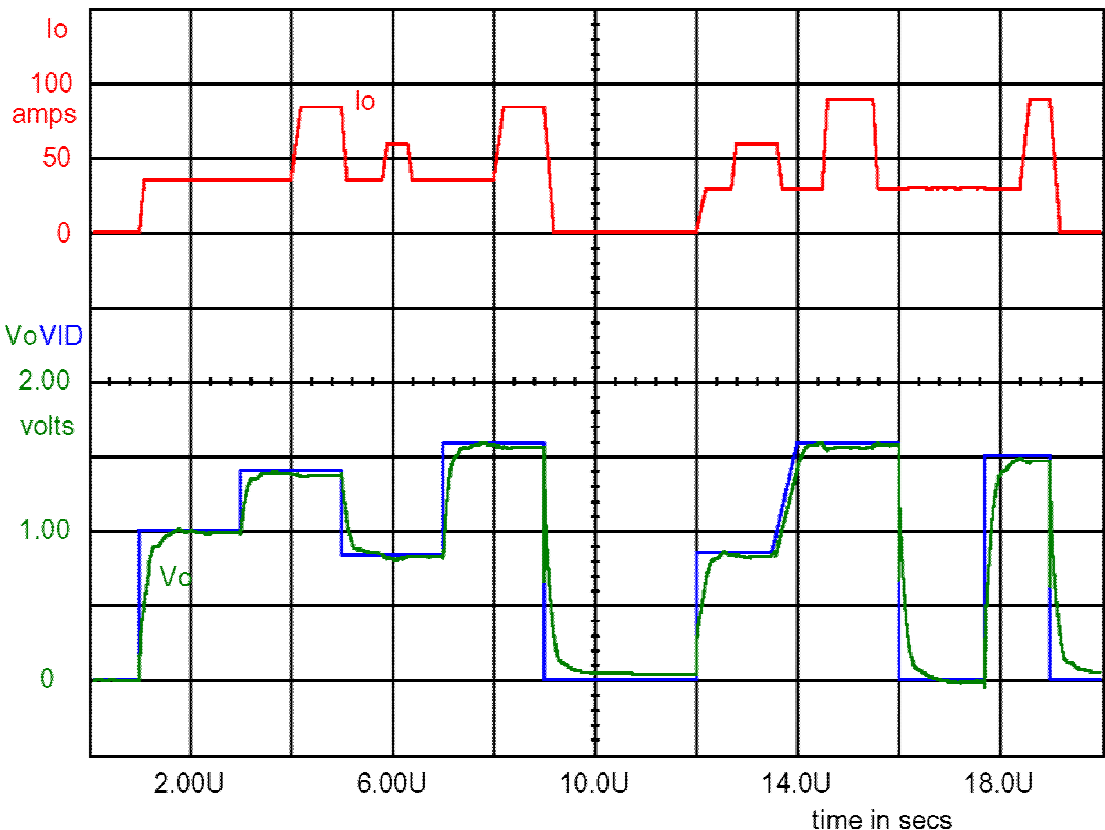- Step, 0 to VID, $< 1 \mu\text{s}$;
Step, VID to 0, $< 2 \mu\text{s}$;
Step, VID to VID', $< 0.5 \mu\text{s}$
- VID slew: $1,500 \text{ mV}/\mu\text{s}$
- No overshoot or undershoot
- Full rated current is immediately available
- Blue curve is digital VID input command.
- Green curve is V_o .
- Red curve is load, I_o .



As compared to a multiphase buck converter, the SCPC has a much lower switching frequency at steady state conditions, or for slow transients (<100 A/us; <20 mV/us).


$$F_s \approx 100 \text{ kHz}$$

The switching is hysteretic, so the switching frequency varies somewhat.


Frequency is for distributed switching. For details, see “Switched Current Power Converters”, Revised 3/13/2006. Chapter 5.0; at <http://eherbert.com>.

- Current sources
- Current switches
- Measurement and control

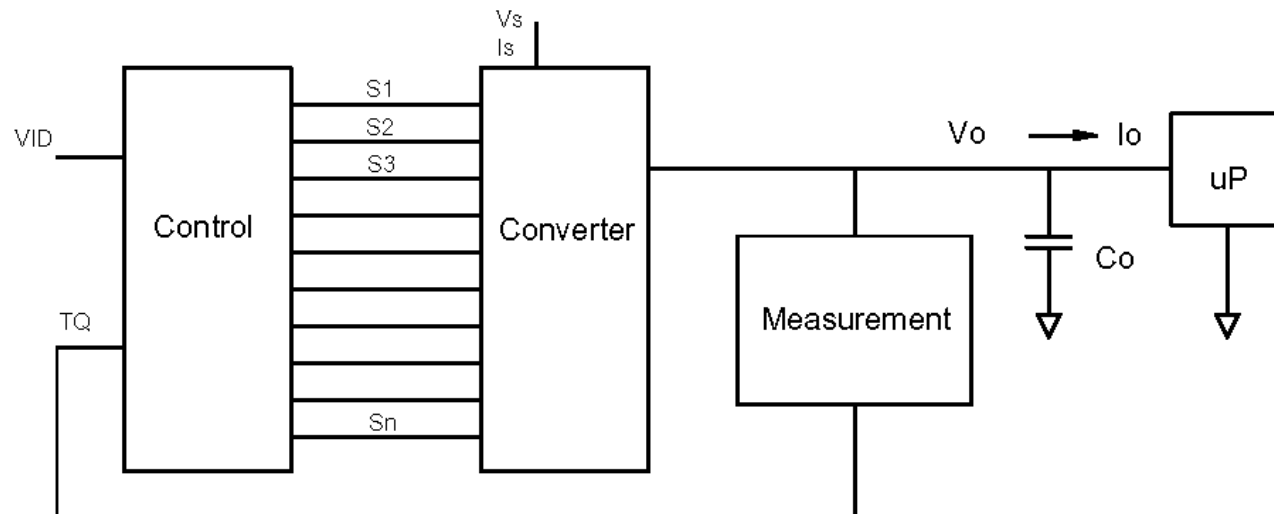Switched Current Power Converter
Block Diagram




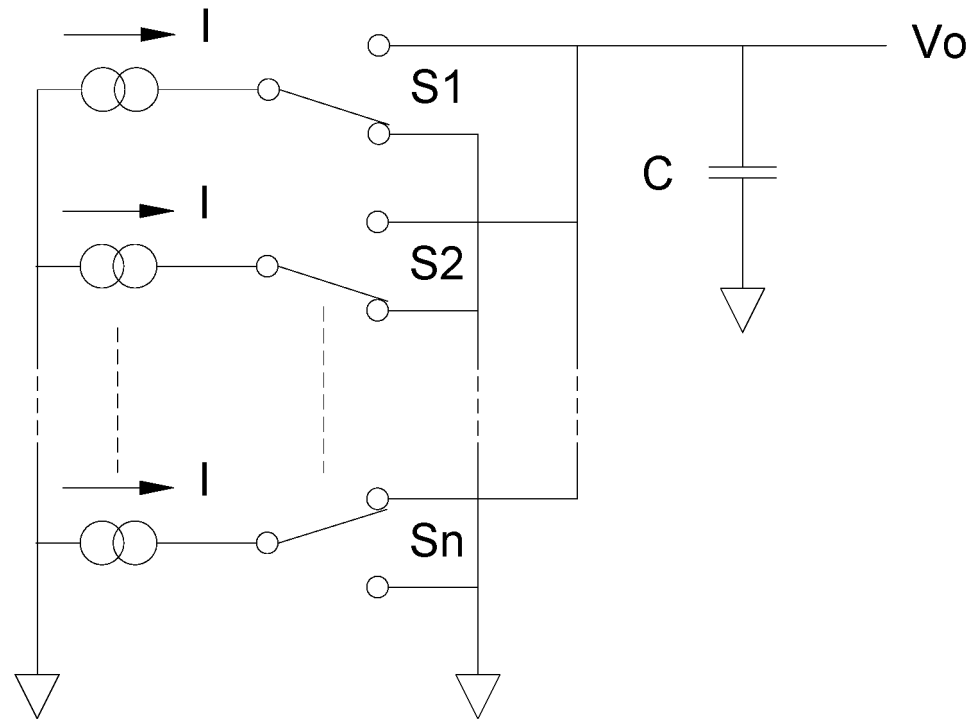- The SCPC controls the output current and steady state voltage by switching currents with solid-state switches.
- *There is no faster converter!*




Voltage measurement

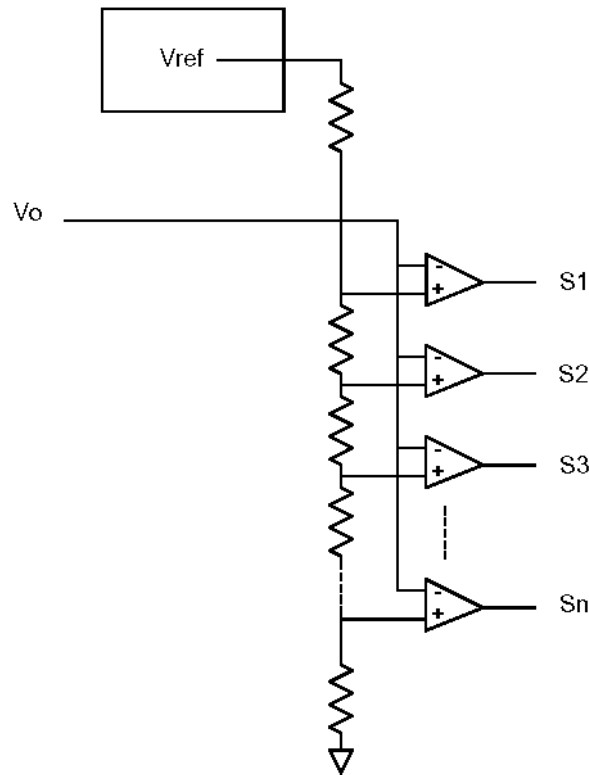- The output voltage is measured using a flash a-d converter.
- *There is no faster voltage measurement!*




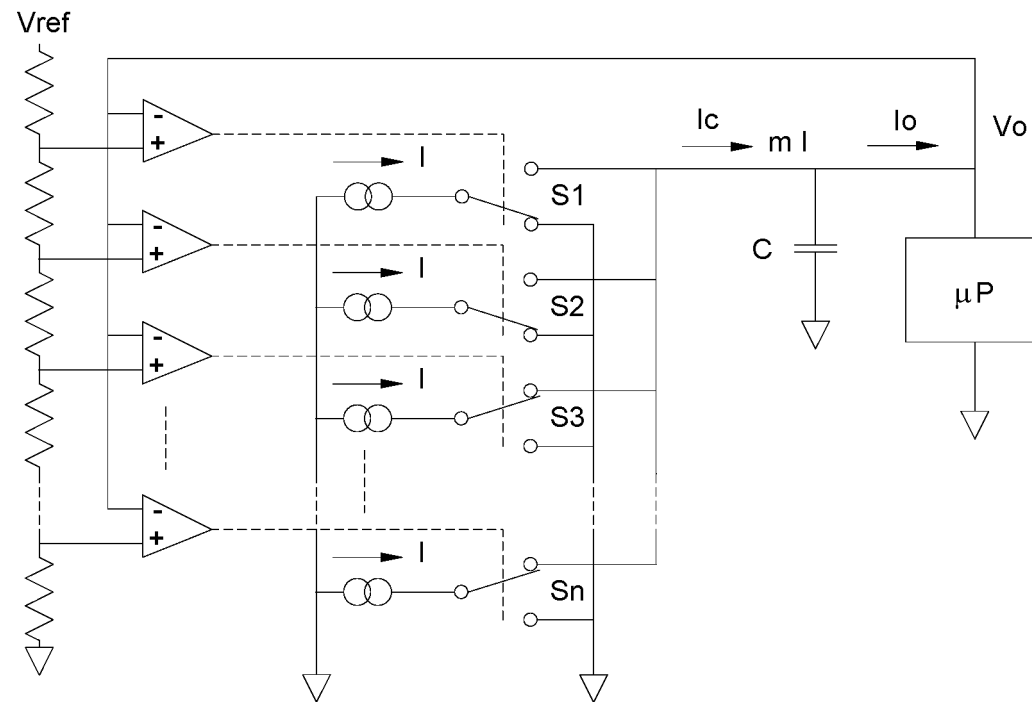- The outputs of the flash a-d directly control the current switches – a true digital control
- *There is no faster control!*




Total charge measurement

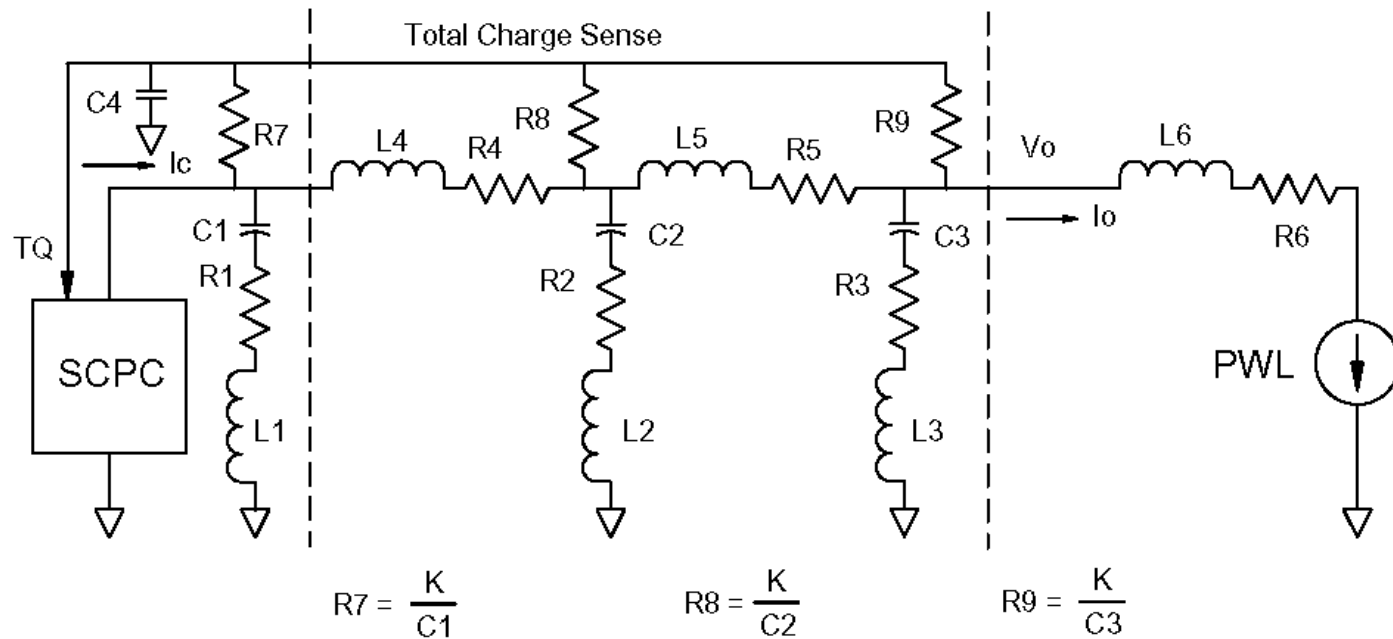- With distributed capacitors and parasitic inductance, the output voltage is not stable enough to use as control input.
- The answer: measure **total charge** as the control input.
- *There is no faster measurement for control!*




- Switched Charge circuits are added to the SCPC for very fast dv/dt , with no changes to the other circuits
- There is no faster upgrade!*

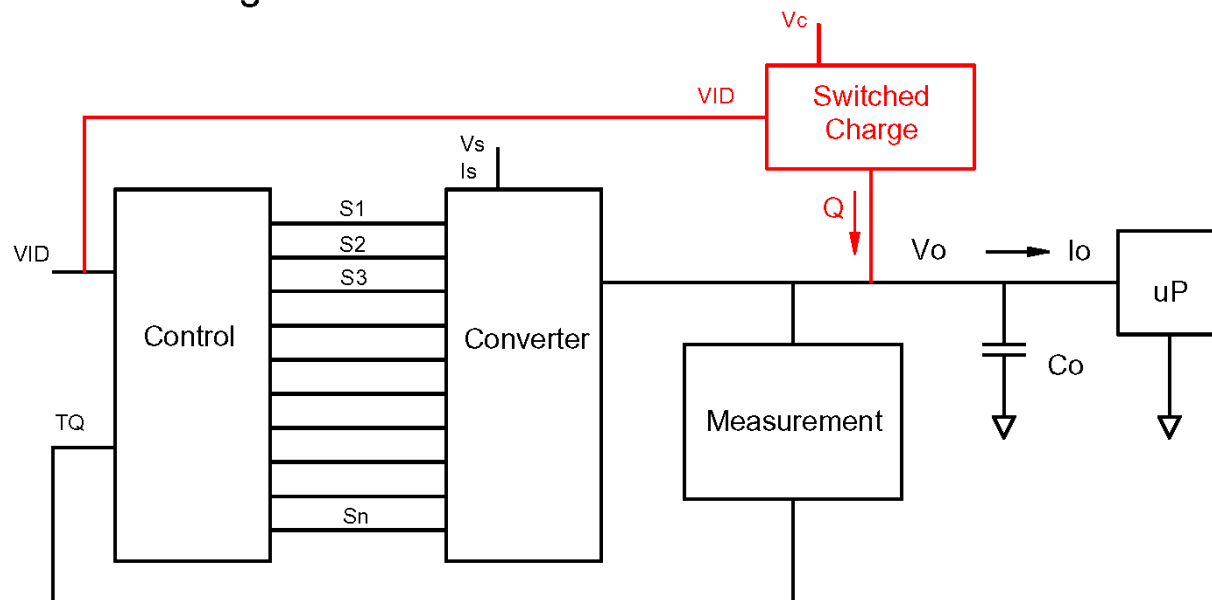Switched Current Power Converter
with Switched Charge Circuits
Block Diagram



Theory: switched charge circuit

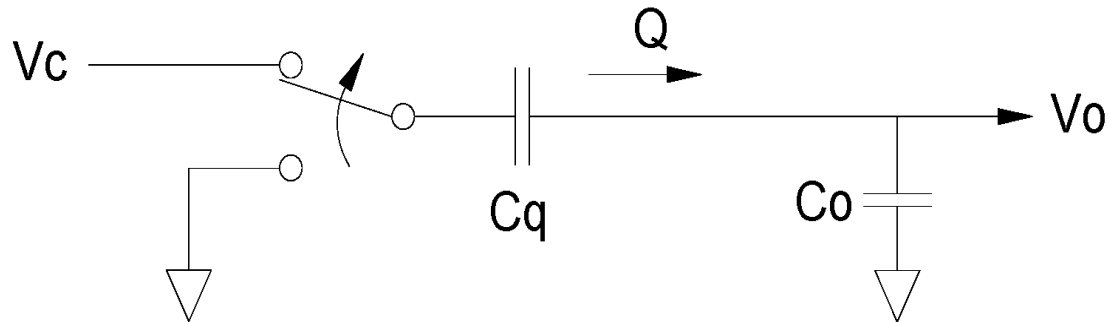
- The output voltage can be stepped very quickly and accurately, up or down, using the Switched Charge Circuit. A precise charge Q is added to the output capacitor C_o .
- *There is no faster way to step the output voltage!*



(Note: The switched charge circuit does not regulate voltage, it only steps the voltage – very rapidly and accurately – with no overshoot. The SCPC current control maintains regulation after the step.)


True digital control!

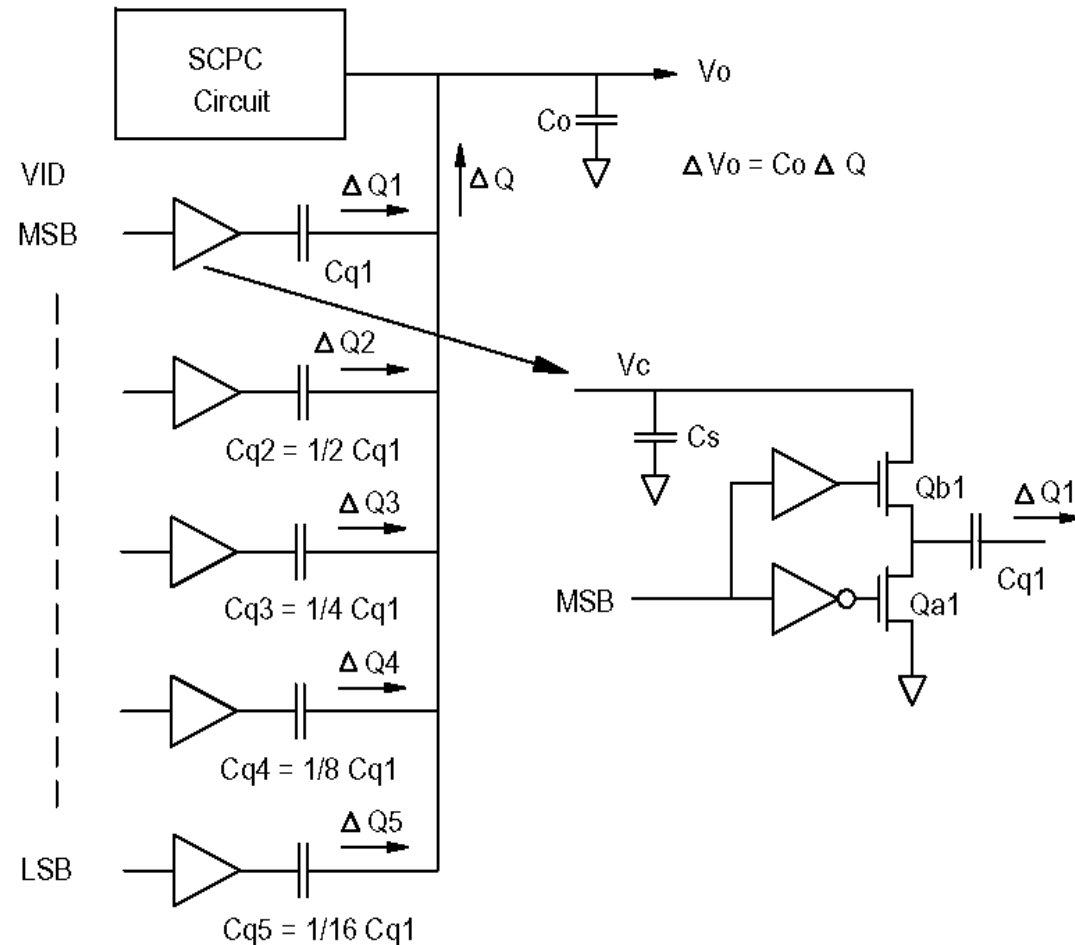- Digital VID controls the binary switched charge circuits
- Digital VID change causes a rapid voltage step ($< 0.5 \mu\text{s}$)
- Output voltage can slew very rapidly (up to $1500 \text{ mV}/\mu\text{s}$) when the digital VID is sequenced




Dual outputs are easy!

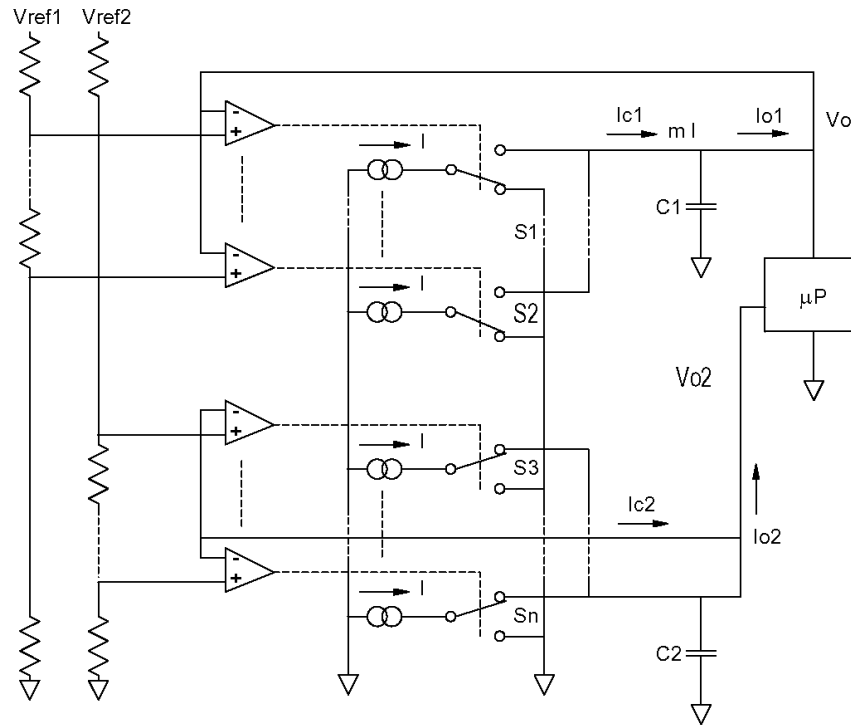- For two voltage outputs for dual core processors,
just divide the SCPC into two halves.
- Each has its own voltage reference (VID) and flash a-d converter



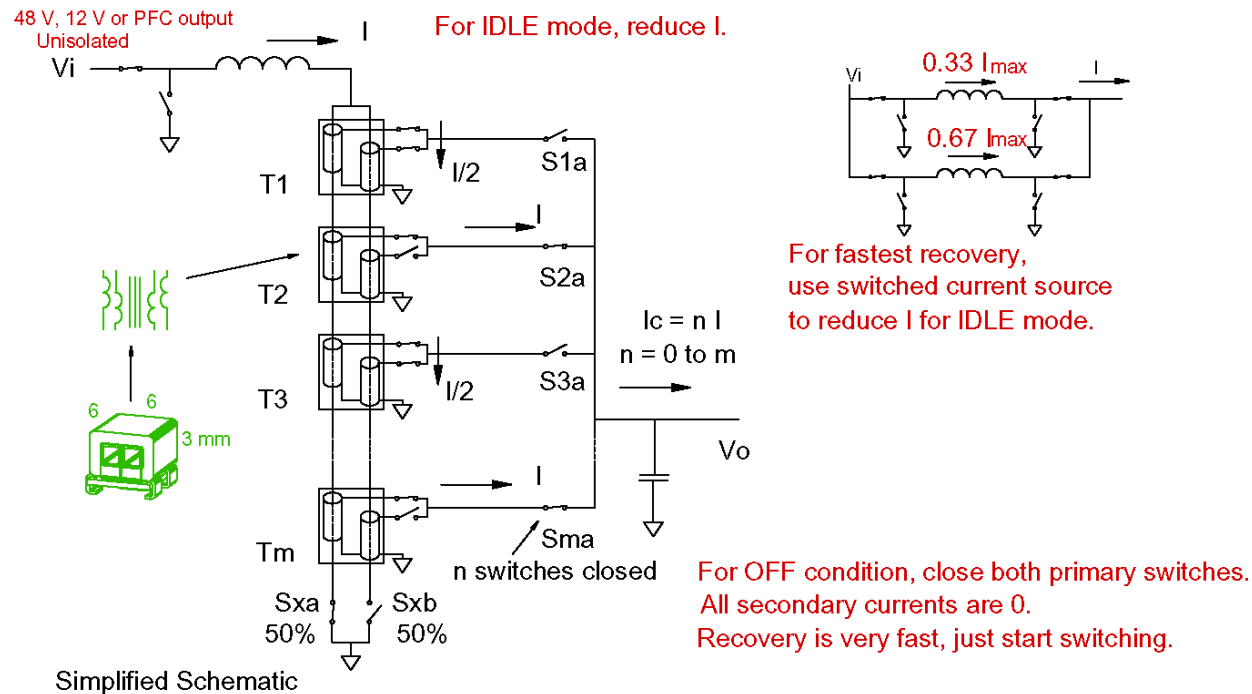
- For higher efficiency in low power modes, the current in the current sources can be reduced:



If the primary current is reduced, fewer switches carry circulating current, and the circulating current is lower.

The logic is simple:

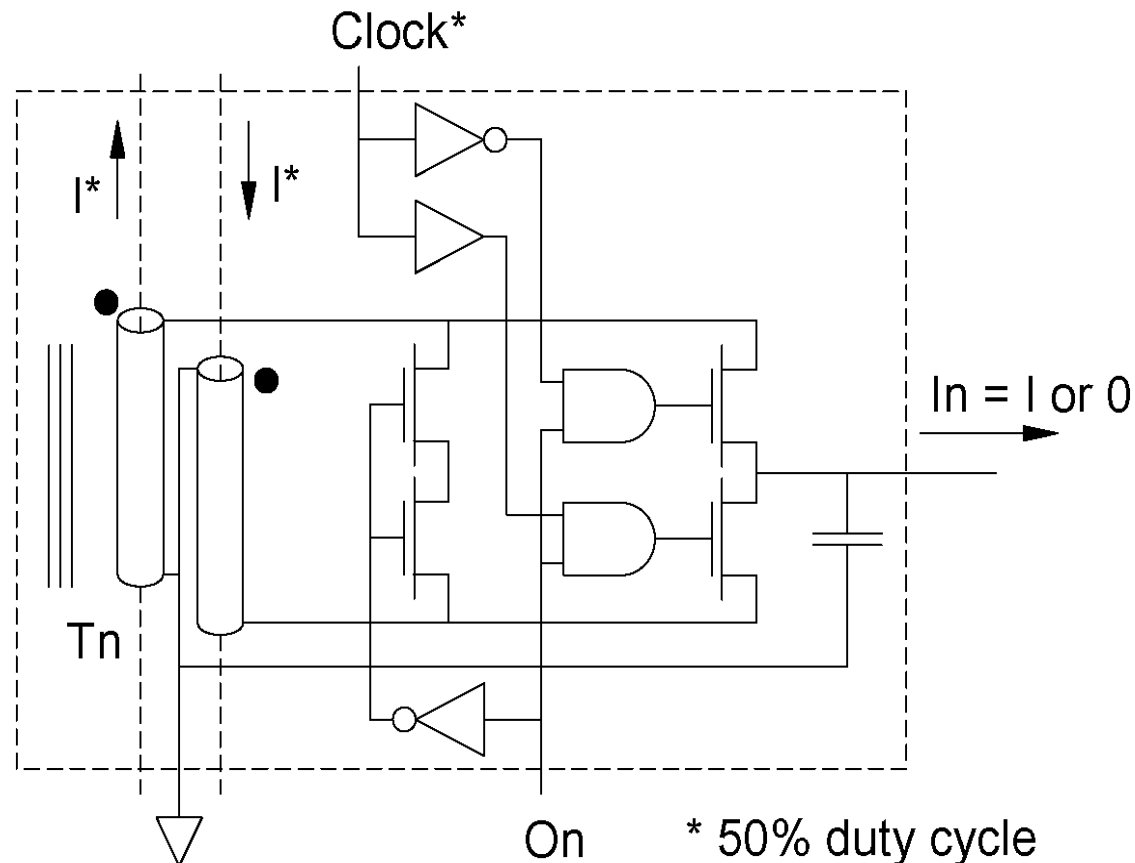- The “Clock” is synchronized to the primary switching.
- The “On” is the flash a-d comparator output.




The **simple power IC** is based on the premise that if all of the MOSFETs in a power IC are the same type, differing only in their active area, then they can all be made at once using nearly the same processing as for an ordinary discrete power MOSFET.

Using this concept, all of the power components of the SCPC secondary circuits can be on **one IC**, if the current is low.


For a VRD (100 A or so), **five identical Ics** are optimum (20 A each).

One additional **logic and control IC** completes the secondary circuits.

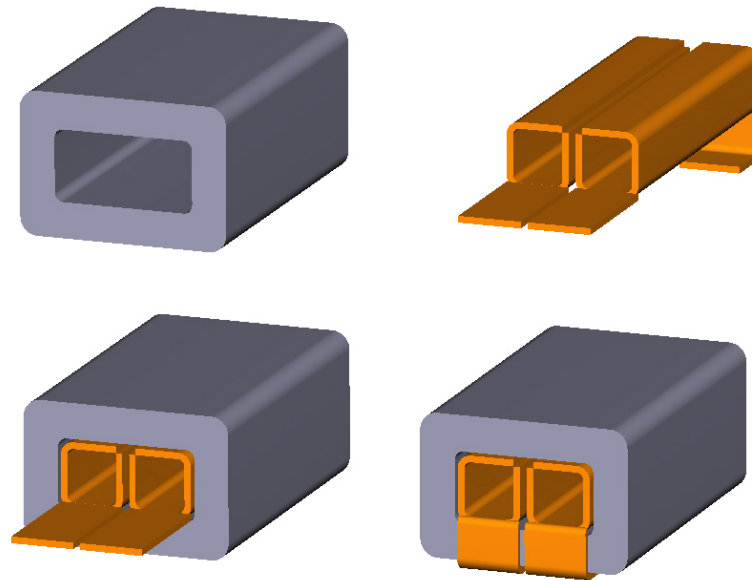- The **coaxial transformer** has two formed metal secondary windings that are inserted into a simple, gap-less pressed **3 x 6 x 6 mm** core. The ends are folded back as self-leads.



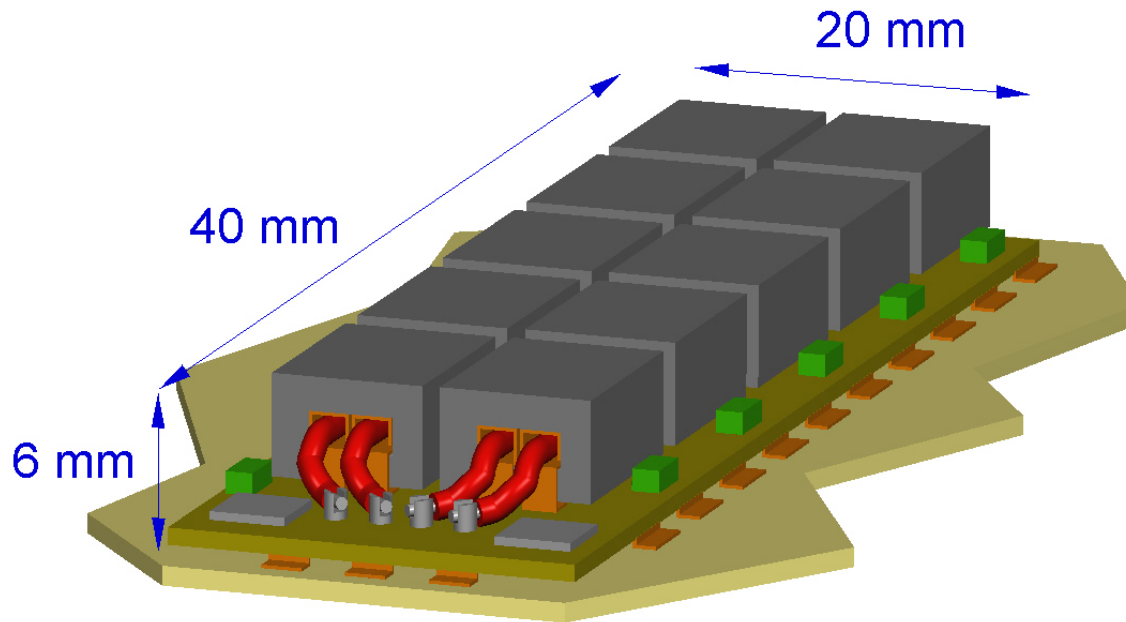The SCPC is assembled on a small daughter board, **6 x 20 x 40 mm**. The master control logic and power ICs mount under the transformers or on the under side. Decoupling capacitors are on the edge.



- The SCPC may be modified to provide multiple outputs, for example, a nine-core processor may have **ten separately controlled voltages**, one for overhead, timing and the cache, and one for each of the nine cores.
- Each output has a separate VID which may be varied dynamically at up to **1,500 V/us**, or it may be turned off (VID, 100% current to 0 V, 0 A) in **1 us**, and it may be turned back on (0 V, 0 A to any VID and any current up to 100%) in **1 us**.

- *Market trends: Faster di/dt ; Faster dv/dt ; More multiple outputs*
- *The SCPC: There is no faster converter*
- *Flash A/D connected directly to current switches: There is no faster control*
- *Total Charge Measurement: There is no faster measurement for control*
- *Adding the Switched Charge Circuit: There is no faster upgrade!*

- This technology is covered in part by U. S. Patent No. 6,121,761, "Fast Transition Power Supply", issued September 19, 2000. Other patents have been allowed are more are pending.
- For more information, see <http://eherbert.com/>

Thank You – Any Questions?